

Wiring Diagram with all PCBs for whole Tonuino with an ESP32 Web-Radio in parallel.

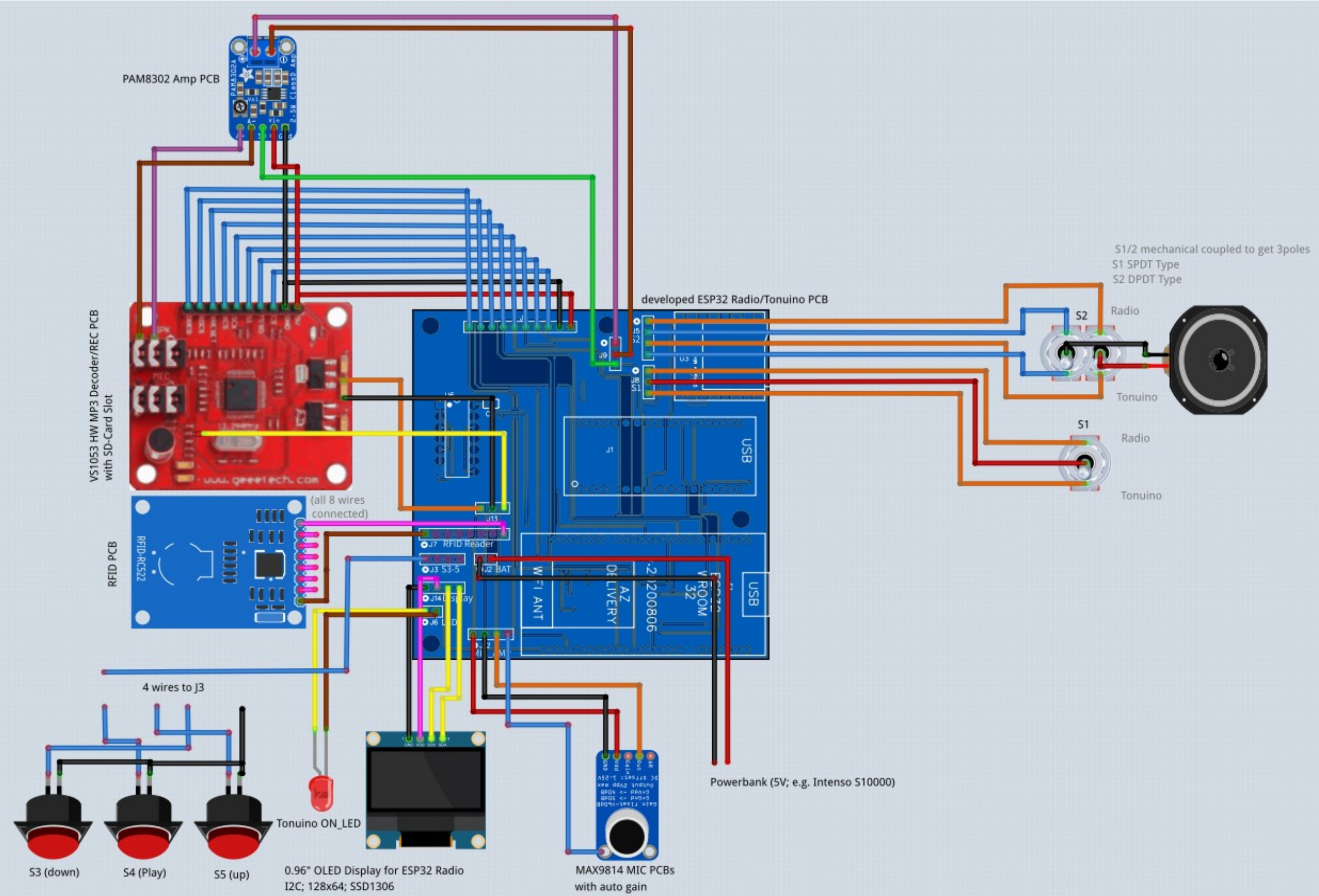


fig 1.1

| | | |
|----------------------------|-----------------------------------|------------|
| TITLE: <div>overview</div> | | REV: 1.0 |
| | Company: Your Company | Sheet: 1/7 |
| | Date: 2020-09-02 Drawn By: uwetaz | |


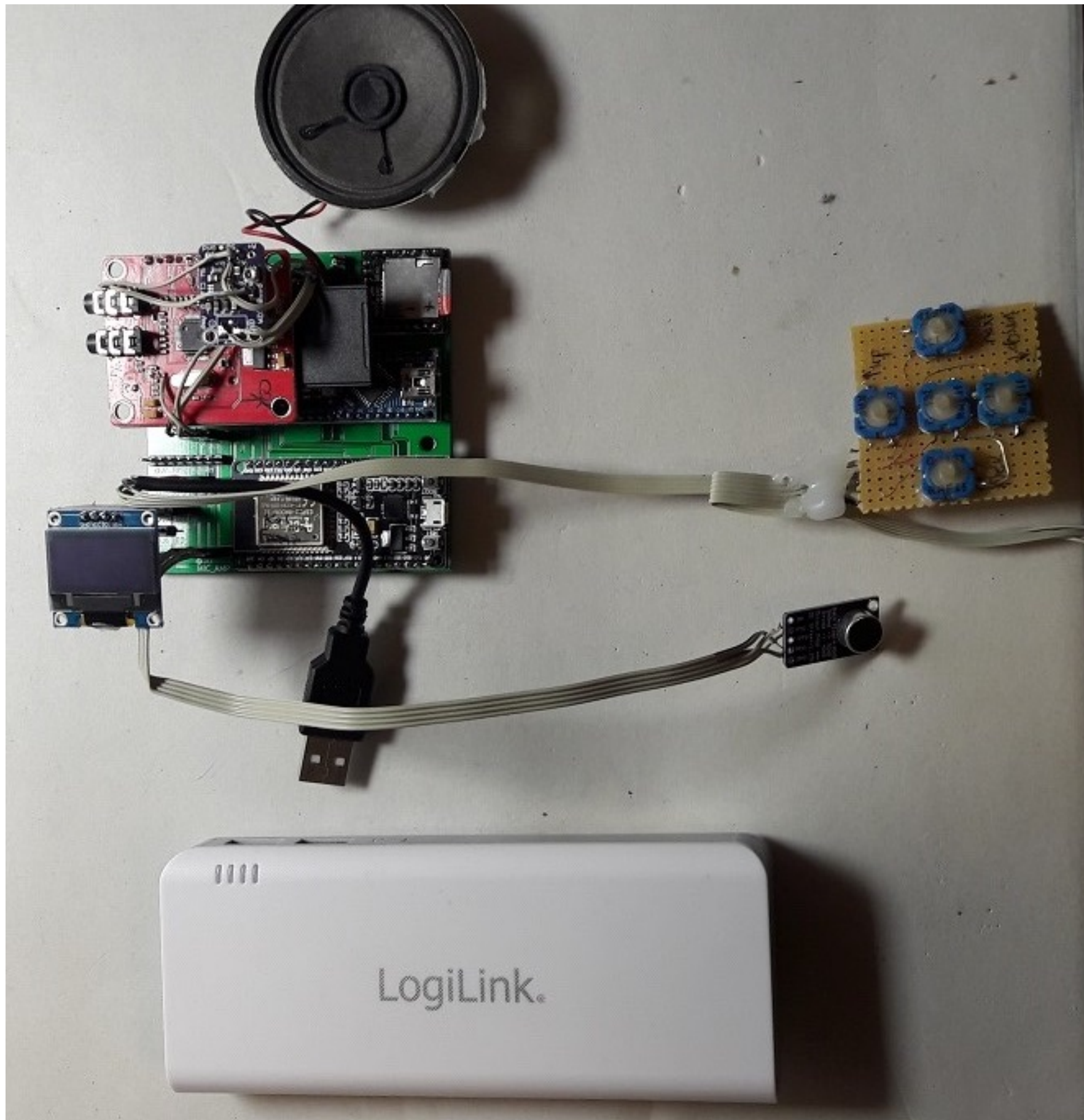
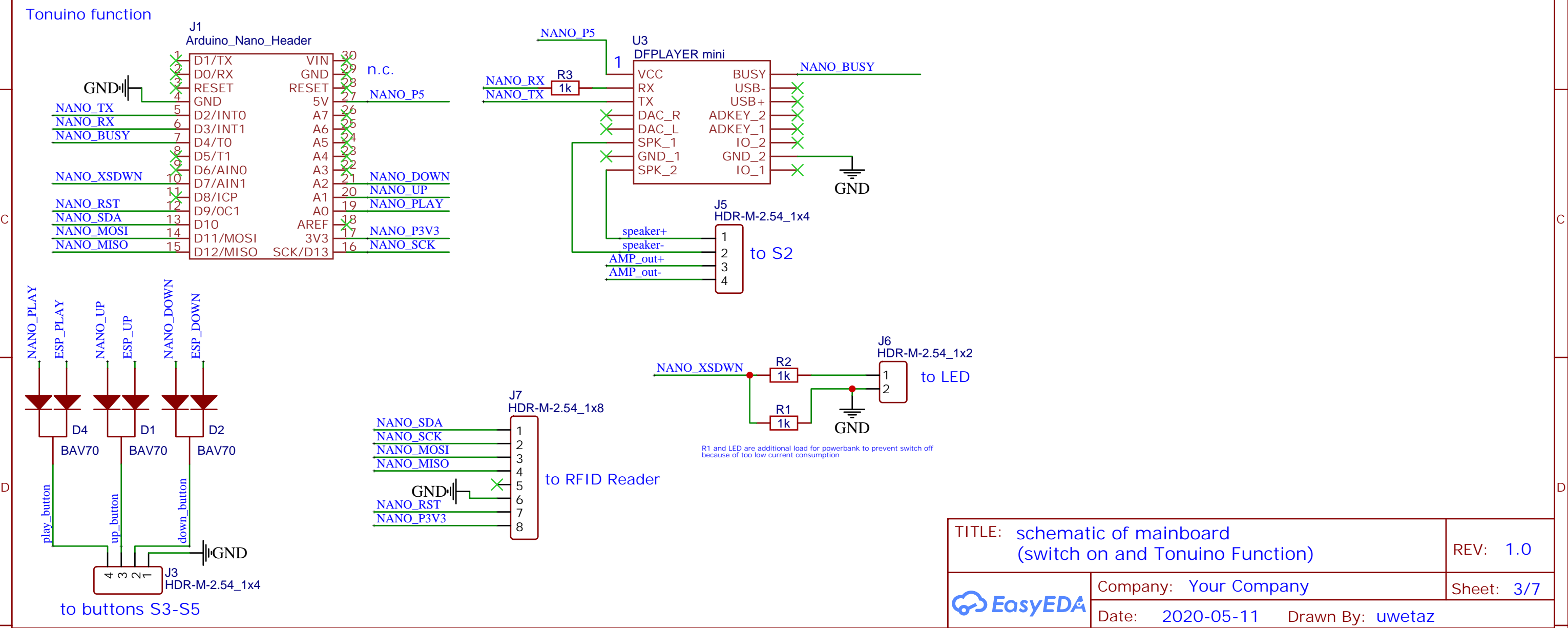


fig 2.1

The following 2 pages describe the mainboard (here green) of ESP32 Radio/Tonuino PCB and mounting to complete system. Btw. the button bread board here has only 3 buttons connected and the RFID reader is not connected. S1/S2 are done temporary with jumpers at mainboard here.

| | | |
|---|-----------------------|------------------|
| TITLE: overview of assembled and connected PCBs | | REV: 1.0 |
| EasyEDA | Company: Your Company | Sheet: 2/7 |
| | Date: 2021-01-15 | Drawn By: uwetaz |

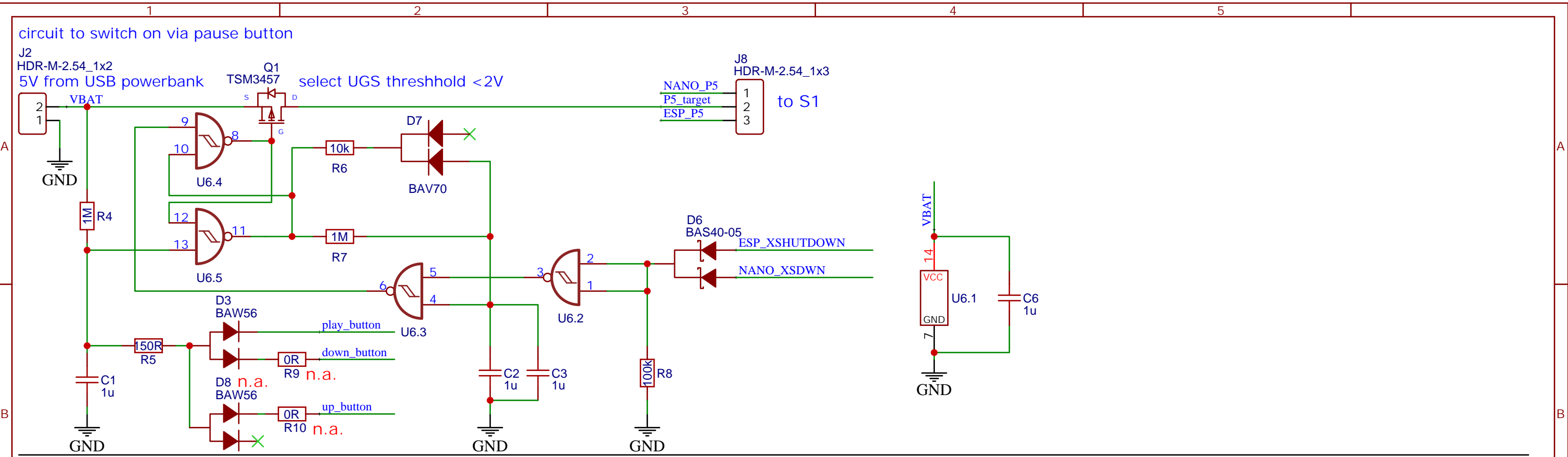

For better understanding regarding the capacitor refer also fig 7.2.

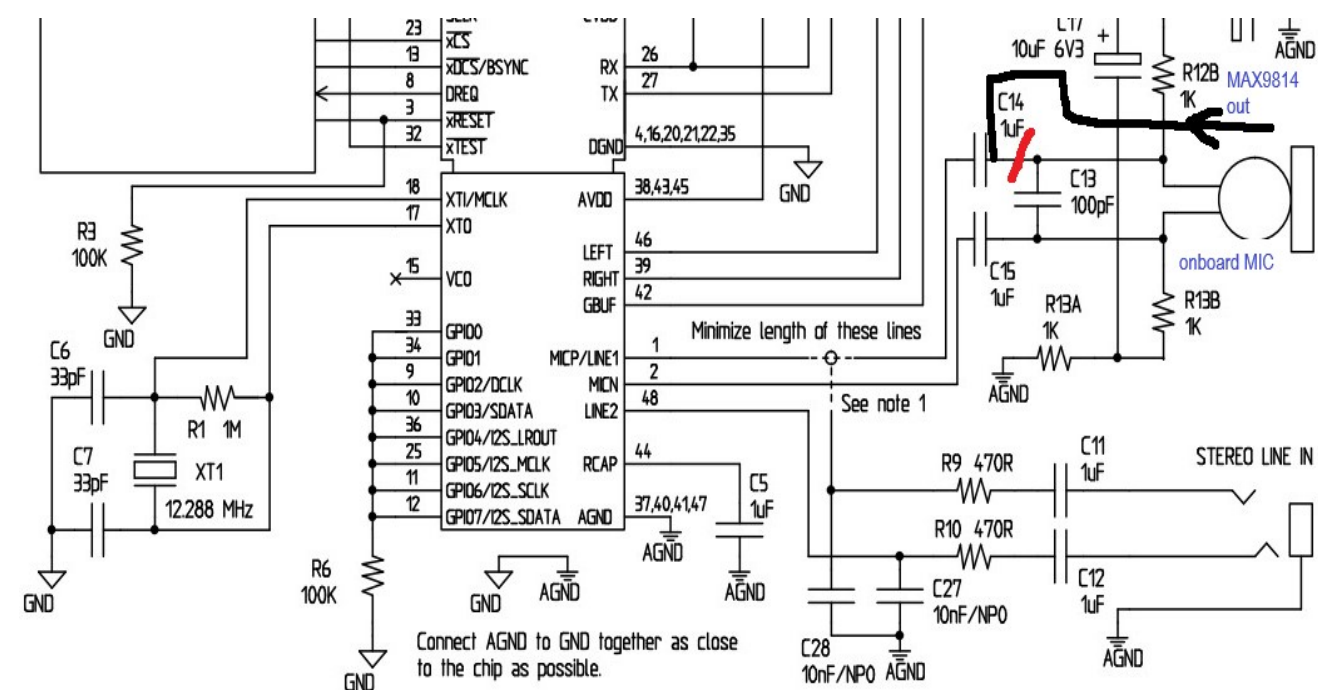


fig 5.1

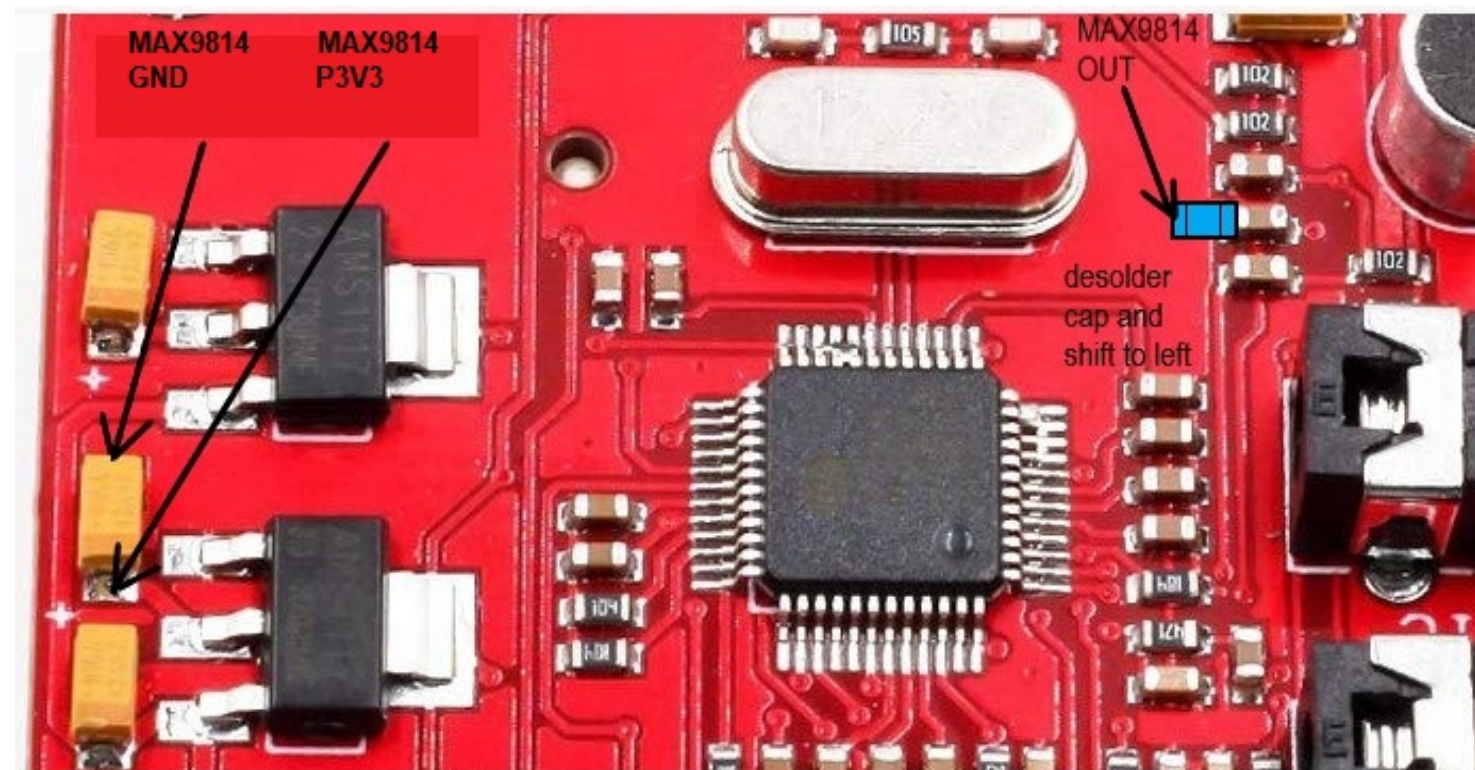


fig 5.2

The LED can be deactivated by desoldering the relevant resistor.

It is only to solder a Resistor at the bottom side to another place.

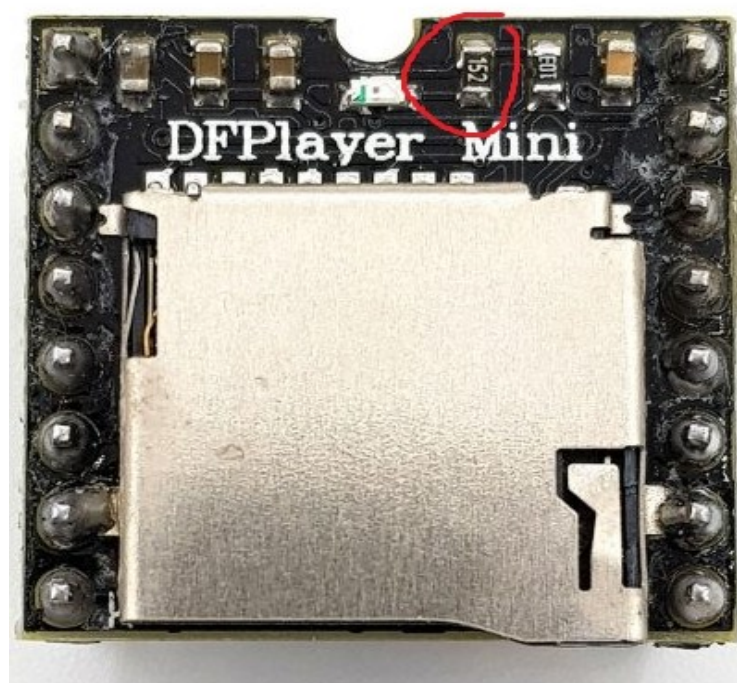


fig 5.3

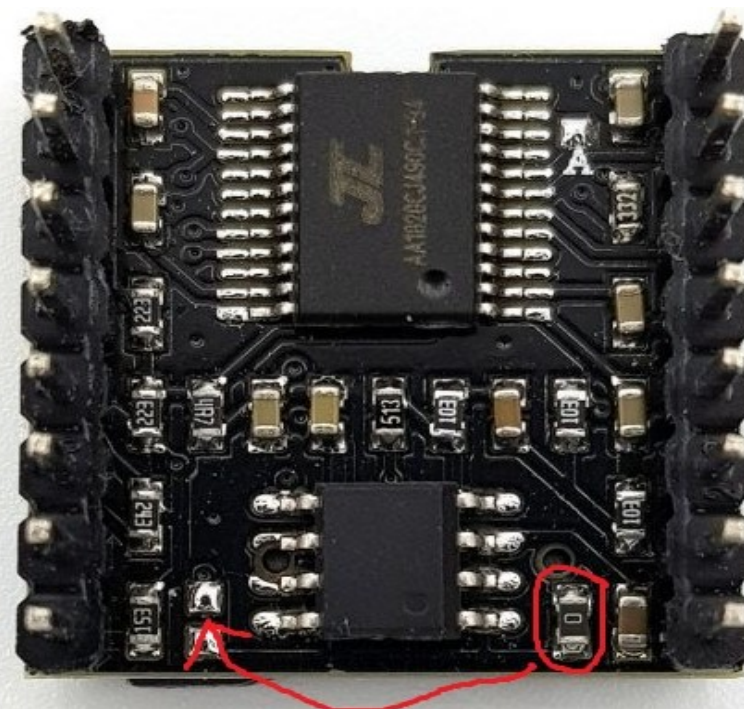


fig 5.4

| | | |
|---|---|--------------|
| TITLE: Modifikations 1/2 | | REV: 1.0 |
|  | Company: Your Company | Sheet: 5/7 |
| | Date: 2020-08-31 Drawn By: uwetaz | |

Modifikations on PAM8302 Amplifier PCB:

1) Short the potentiometer to get symmetric input and eliminate noise by WLAN of ESP.
Or you connect A+ after the potentiometer as here.

2) desolder 10k Pullup at XSD Signal (here not done yet)

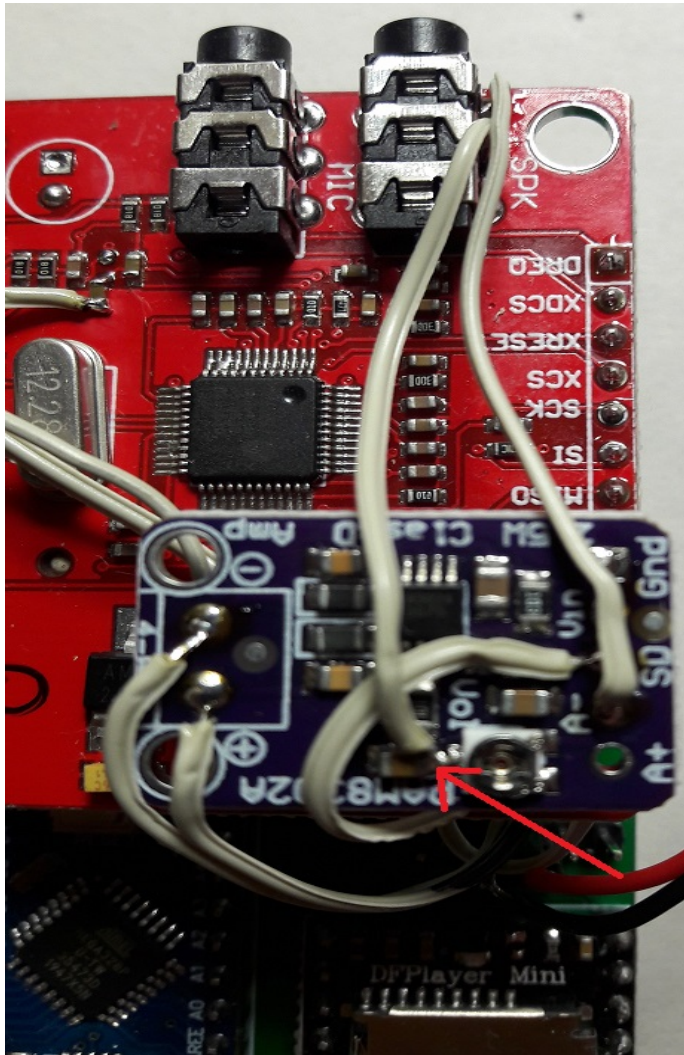


fig 6.1

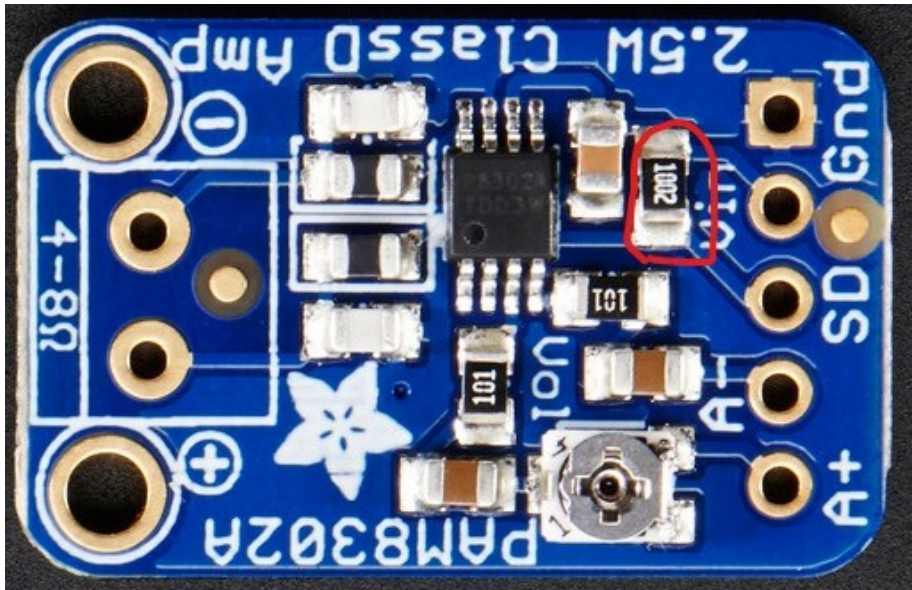


fig 6.2

optional Modification on MAX9814 Microphon Amp Board for a shutdown function (to spare 3mA at 3.3V):

- cut Net on Pin 2 at PCB
- make a 47k Pullup to Pin2 and route to a good contact place
- this spares 3mA on 3,3V Side if not recording
- 1uF is connected at V+ and GND (at top side here)

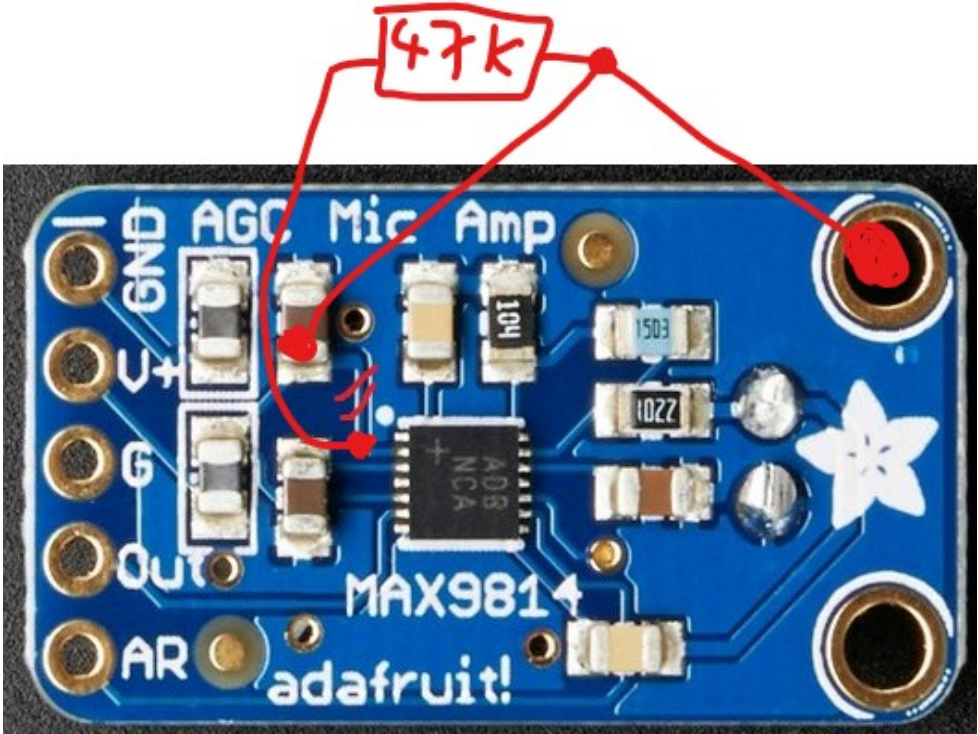


fig 6.3



fig 6.4

| | | |
|--------------------------|-----------------------|------------------|
| TITLE: Modifikations 2/2 | | REV: 1.0 |
| EasyEDA | Company: Your Company | Sheet: 6/7 |
| | Date: 2020-09-02 | Drawn By: uwetaz |

- 1

2

3

4

5
- 1) It is helpfull to test VS1053 PCB and Display after flashing the ESP32 board and temporary wiring as here shown.
You have only connect earphones to SPK output.

2) modify the bought PCBs (Nano, DF-Player, RFID Reader, ESP-Board, VS1053 PCB, PAM8302 PCB and MAX9814 PCB) according page 5/6
At Arduino Nano, RFID PCB and ESP32 Dev Board only the LED resistors can optional be desoldered to reduce current consumption (here not shown).

3) Assemble the PCB (SMDs first, then the rest)

4) Assemble Arduino Nano, DF-Player, ESP Board and all other THT stuff.

5) mounting and wiring of VS1053 PCB and then PAM8302 PCB

6) wiring/connecting the other peripherals acording page 2

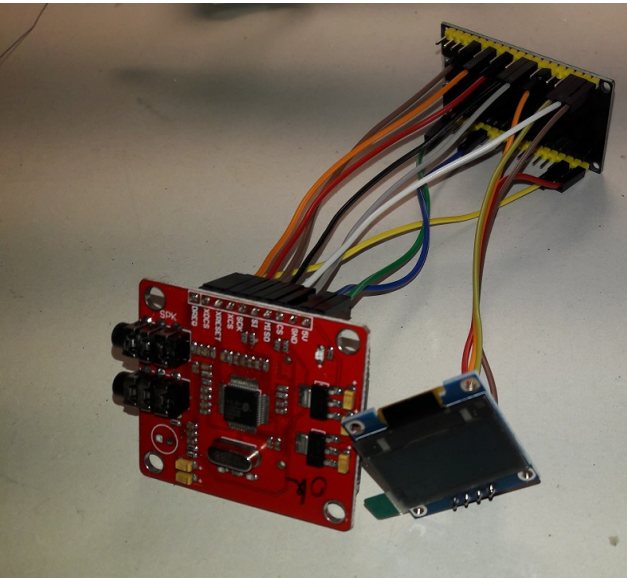


fig 7.1 temporary wiring of ESP32 Part

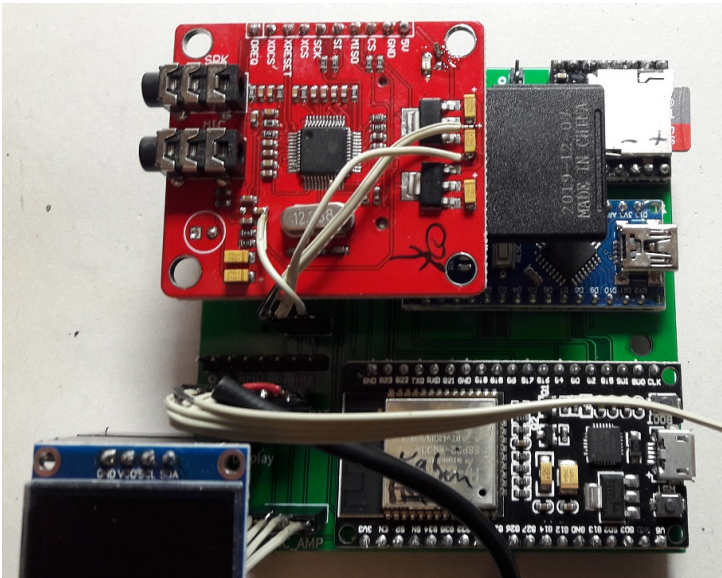


fig 7.2 wiring of VS1053 PCB to J13

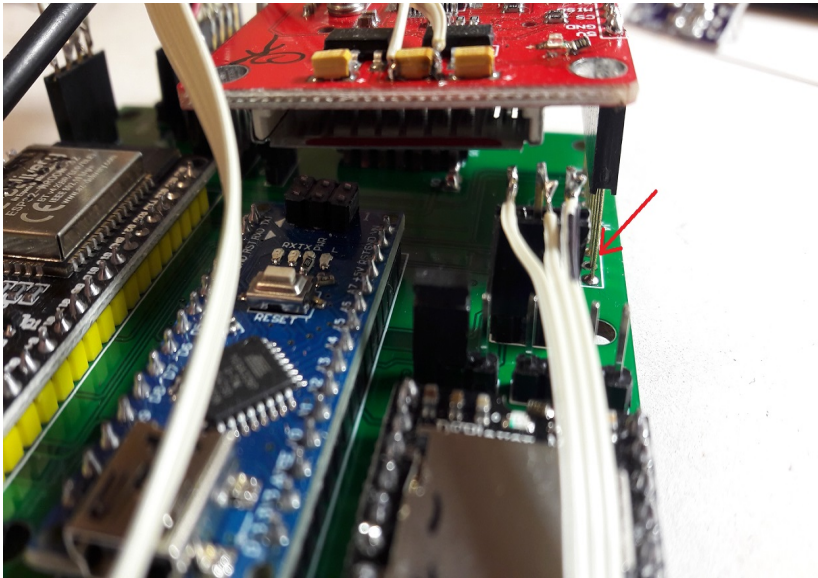


fig 7.3
using 2,54mil 10 pin female header J4 with long pins for right position of VS1053 PCB
if the SD card holder of VS1053 PCB colidate with the arduino Nano IPS header you can cut off them as here shown.

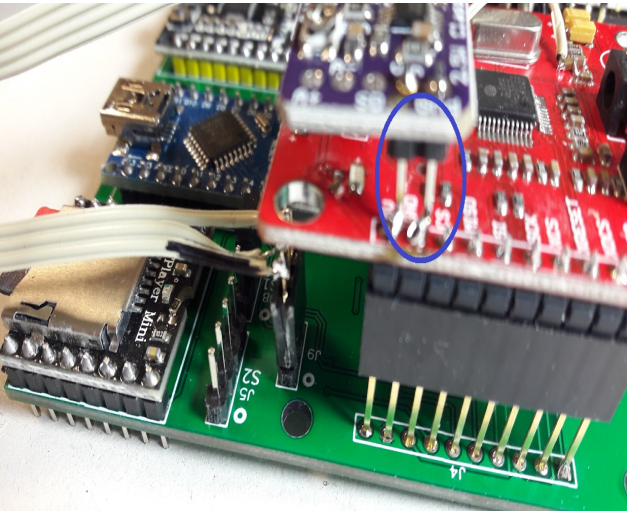


fig 7.4 mounting of PAM8302 PCB with 2pin header at VS1053 PCB

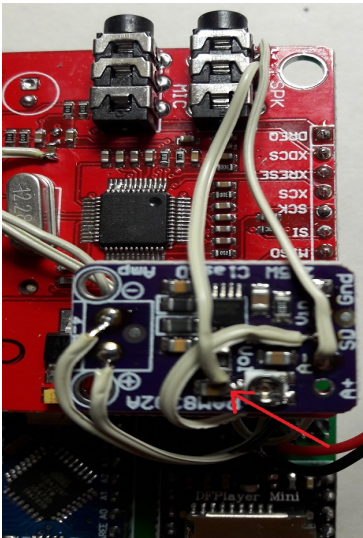


fig 7.5 wiring of PAM8302 to J9 and VS1053 audio out

| | | |
|-----------------------|-----------------------|------------------|
| TITLE: assembly hints | | REV: 1.0 |
| EasyEDA | Company: Your Company | Sheet: 7/7 |
| | Date: 2021-01-15 | Drawn By: uwetaz |